

COMPUTER SCIENCE TRIPOS Part IA – 2023 – Paper 2

1 Digital Electronics (ijw24)

- (a) Simplify the following Boolean function into both sum of products and product of sums forms, taking into account the don't care terms $A.B$ and $A.C$

$$F(A, B, C, D) = \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + \bar{A}.\bar{B}.D + \bar{A}.C.\bar{D}$$


[5 marks]

- (b) Using a Karnaugh Map, simplify the following Boolean function into sum of products form

$$G(A, B, C, D) = (\bar{A} + \bar{B} + C).(B + C + \bar{D}).(A + \bar{B} + D).(\bar{A} + B + \bar{D}).(\bar{B} + C + D)$$

[3 marks]

 - (c) For the following circuit, assume that all the logic gates have an equal value of non-zero propagation delay and that $X = 0$ and $Y = 0$



- (i) With the aid of a timing diagram, show that a static hazard is present at output P when input Z changes from 0 to 1.
- (ii) With the assistance of a Karnaugh Map, show how the static hazard identified in Part (c)(i) can be eliminated.

[7 marks]

- (d) (i) Show how the following Boolean function may be implemented using an 8:1 multiplexer. Use variable X as the most significant bit of the multiplexer selector inputs

$$M(X, Y, Z) = \bar{X}.\bar{Y}.Z + \bar{X}.Y.Z + X.\bar{Y}.\bar{Z} + X.\bar{Y}.Z$$

- (ii) Show how the function in Part (d)(i) may alternatively be implemented using a 2:1 multiplexer and a NOT gate. Assume that complemented input variables are *not* available.

[5 marks]

2 Digital Electronics (ijw24)

(a) D type flip-flops are to be used to implement a synchronous counter having an output sequence 0, 1, 2, 3, 4, 5, 0, ... (decimal).

(i) Determine the next state combinational logic required for the D type flip-flops.

(ii) Show whether or not the counter self-starts.

[8 marks]

(b) A finite state machine is represented by the following state table:

Current state (Q)	Next state (Q')					Output (Z)
	$XY =$	00	01	10	11	
A		A	F	C	B	0
B		A	B	D	H	1
C		G	B	C	D	0
D		C	F	D	D	1
E		G	A	E	D	1
F		F	F	G	B	0
G		G	B	G	E	0
H		F	B	E	H	1

(i) Determine the equivalent states using the state equivalence/implication table approach.

(ii) Show the reduced state table.

[9 marks]

(c) Consider two D type flip-flops operating in a synchronous configuration. The input of the second flip-flop, D_2 , is connected to the output of a combinational logic block, and one of the inputs to the combinational logic block is connected to the output, Q_1 , of the first flip-flop.

For both flip-flops, the minimum set-up time $t_{su,min} = 20$ ns, the minimum hold time $t_{h,min} = 5$ ns, and the maximum propagation delay $t_{pc,max} = 40$ ns. The maximum propagation delay of the combinational logic block from Q_1 to D_2 is $t_{pd,max} = 49$ ns.

(i) Determine the maximum clock frequency for this circuit.

(ii) How could this be increased without changing the flip-flops?

[3 marks]